
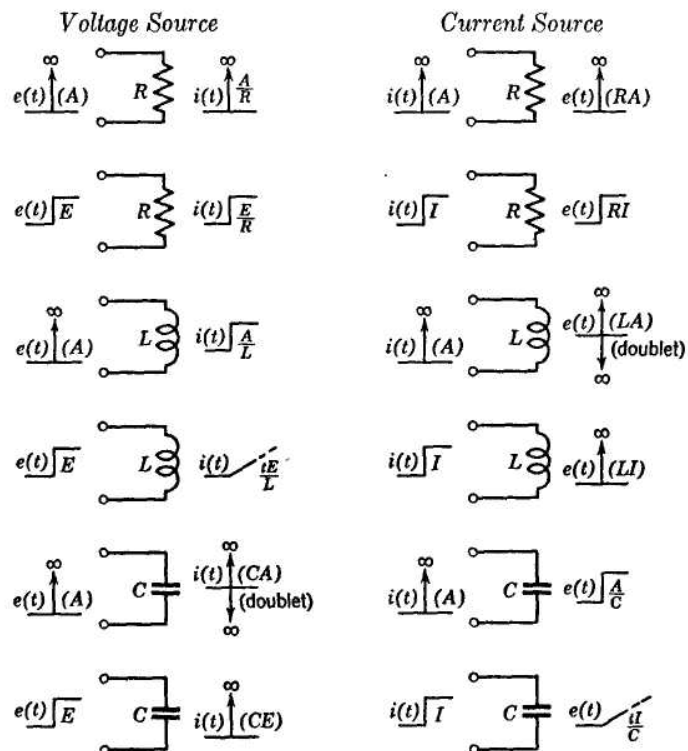





SUMMARY REGARDING THE TRANSIENT RESPONSE
OF ONE-, TWO-, AND THREE-ELEMENT COMBINATIONS

A *Single Elements*






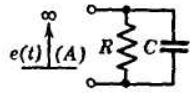


C Two Elements— R, C 





i_R, i_C same as
in part (A)

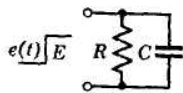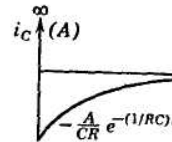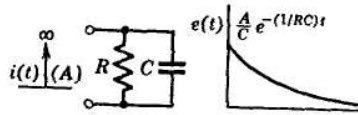





i_R, i_C same as
in part (A)

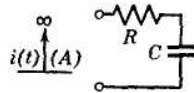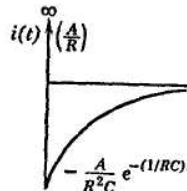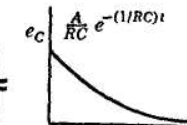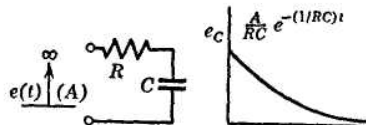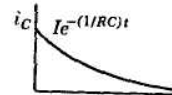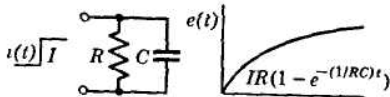


e_R, e_C same as
in part (A)

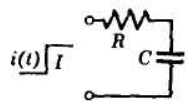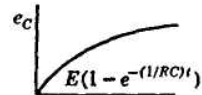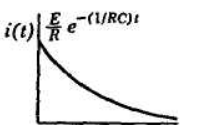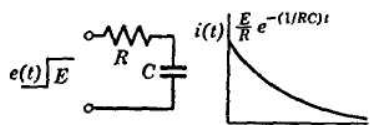

e_R, e_C same as
in part (A)

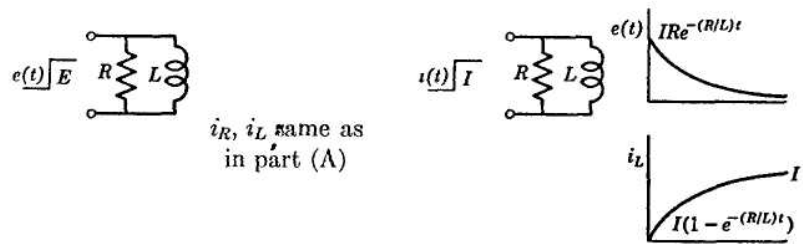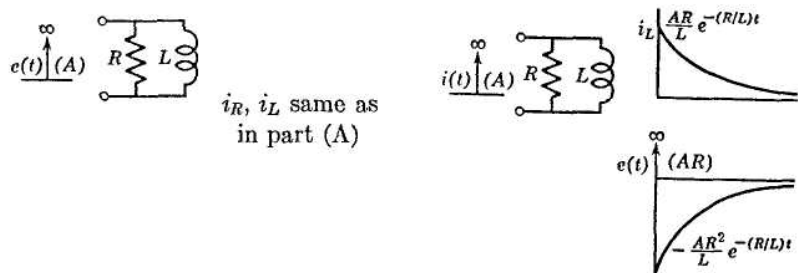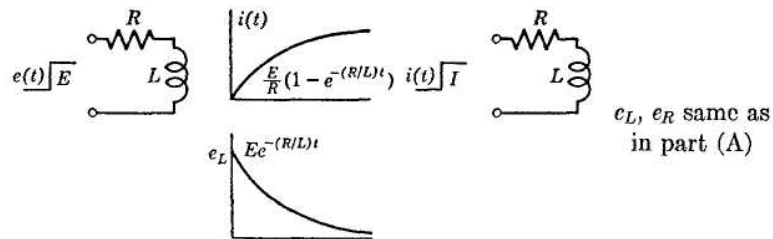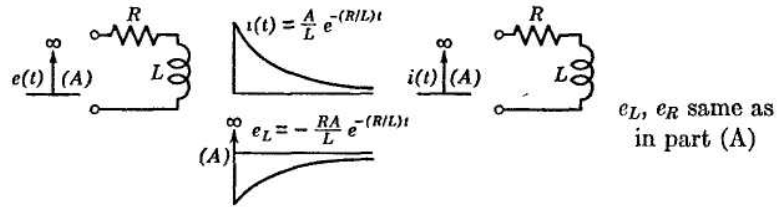B Two Elements— R, L 

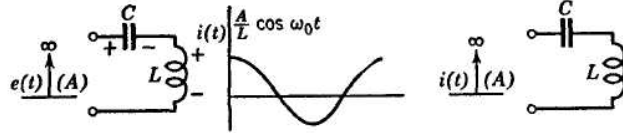
D Two Elements— L, C $\omega_0 = 1/\sqrt{LC}$




$$e_L = L \frac{di}{dt} = A u_0(t) - A \omega_0 \sin \omega_0 t$$

$$e_C = \frac{1}{C} \int i dt = A \omega_0 \sin \omega_0 t$$

e_C, e_L same as in part (A)

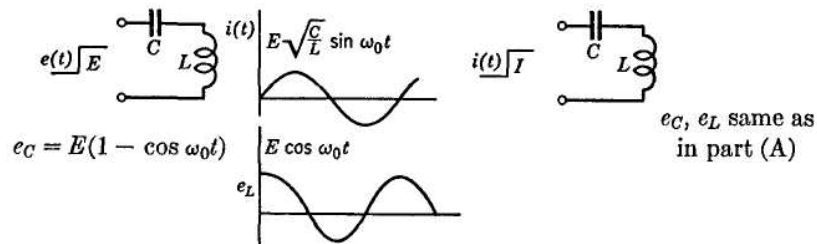


e_C, e_L same as in part (A)

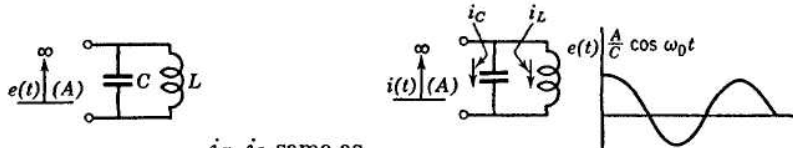

i_C, i_L same as in part (A)

$$i_C = C \frac{de}{dt} = A u_0(t) - A \omega_0 \sin \omega_0 t$$
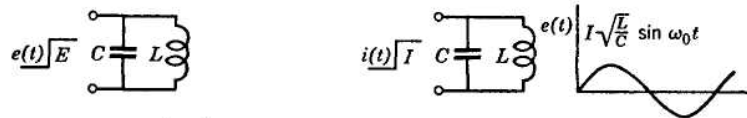
$$i_L = \frac{1}{L} \int e dt = A \omega_0 \sin \omega_0 t$$




i_C, i_L same as in part (A)

$$i_L = I(1 - \cos \omega_0 t)$$

E Three Elements— R, L, C
 $(\omega_0 > \alpha)$

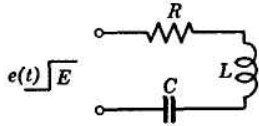
$$\omega_0 = \frac{1}{\sqrt{LC}} \quad \alpha = \frac{R}{2L} \quad \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$




$$i(t) = E \sqrt{\frac{C}{L}} \frac{\omega_0}{\omega_d} e^{-\alpha t} \sin \omega_d t$$

when $\alpha \ll \omega_0$
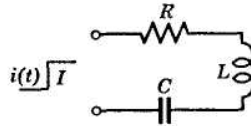
$$i(t) \approx E \sqrt{\frac{C}{L}} e^{-\alpha t} \sin \omega_0 t$$




e_L, e_R, e_C as shown
in part (A)

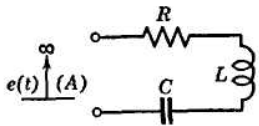


$$i(t) = \frac{A}{L} \frac{\omega_0}{\omega_d} e^{-\alpha t} \cos \left(\omega_d t + \cos^{-1} \frac{\omega_d}{\omega_0} \right)$$

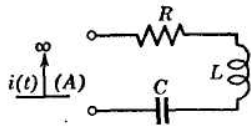
when $\alpha \ll \omega_0$; $i(t) \approx \frac{A}{L} e^{-\alpha t} \cos \omega_0 t$



e_L, e_R, e_C as shown
in part (A)

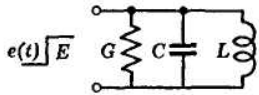


i_G, i_L, i_C as shown
in part (A)

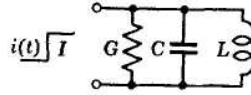

$$e(t) = I \sqrt{\frac{L}{C}} \frac{\omega_0}{\omega_d} e^{-\alpha t} \sin \omega_d t$$

when $\alpha \ll \omega_0$

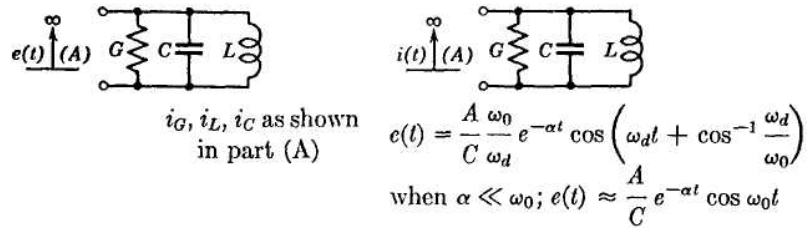
$$e(t) \approx I \sqrt{\frac{L}{C}} e^{-\alpha t} \sin \omega_0 t$$



Note: When $\alpha \ll \omega_0$, it is necessary only to insert $e^{-\alpha t}$ as a multiplier to the results of part (D).


F Initial Conditions

1 Initial voltages on condensers

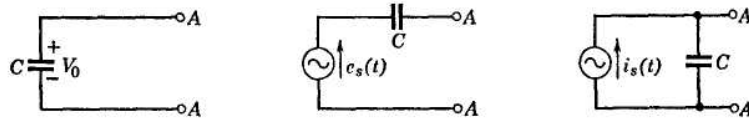

Charged condenser $e_s(t) = V_0 u_{-1}(t)$ in series $i_s(t) = C V_0 u_0(t)$ in parallel

2 Initial currents in coils

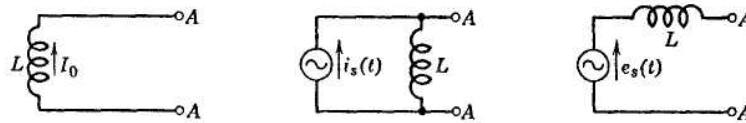


Initial current $i_s(t) = I_0 u_{-1}(t)$ in parallel $e_s(t) = L I_0 u_0(t)$ in series


If other sources are present in the circuit solve by superposition.

PROBLEMS

1. For the circuit shown below, determine $e(t)$ and $i(t)$ (a) for $i_s(t) = u_0(t)$, (b) for $i_s(t) = u_{-1}(t)$.

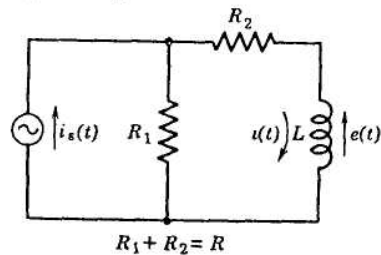


PROB. 1.

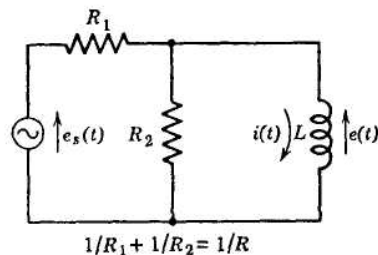


PROB. 2.

2. For the circuit shown above, determine $e(t)$ and $i(t)$ (a) for $e_s(t) = u_0(t)$, (b) for $e_s(t) = u_{-1}(t)$.
 3. Given $i_s(t) = u_{-1}(t)$. Determine $e(t)$ and $i(t)$.

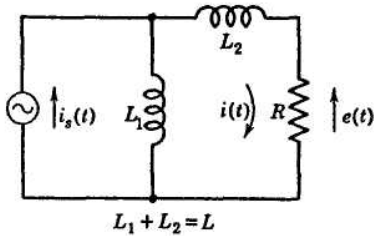


PROB. 3.

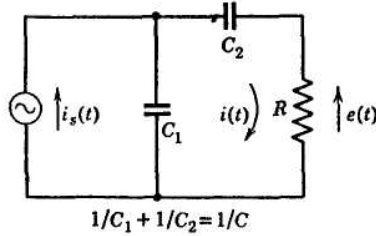


PROB. 4.

4. Given $i_s(t) = u_0(t)$. Determine $e(t)$ and $i(t)$.
 5. Given $e_s(t) = u_0(t)$. Determine $e(t)$ and $i(t)$.

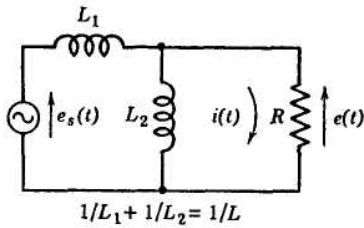


PROB. 5.

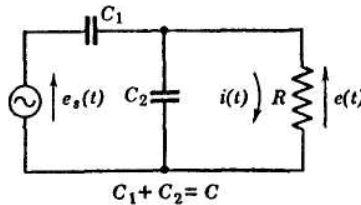


PROB. 6.

6. Given $e_s(t) = u_{-1}(t)$. Determine $e(t)$ and $i(t)$.
 7. For the circuit shown below, R_1 represents the leakage resistance of the condenser of capacitance C . What is the equation for the charge on the condenser as a function of time after the switch K is closed?

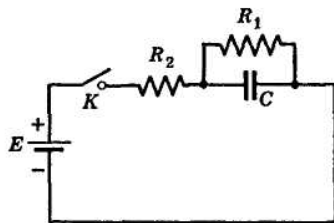

PROB. 7.

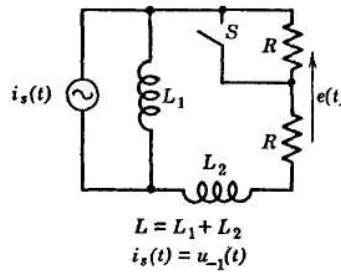

PROB. 9.

8. Which pairs of the circuits in Probs. 1 to 6 inclusive are potential duals? Using this information, check your answers to these problems.
 9. Switch S is closed for $0 < t < L/R$ and is open during the interval $L/R < t < \infty$. Find analytic expressions for the voltage $e(t)$ valid for $0 < t < L/R$ and again for $L/R < t < \infty$.